

Electricity and Electrical Circuits: Current, Voltage, and Resistance

1. Which of the following best describes electric current?

- The amount of energy stored in a battery
- The flow of electric charge through a conductor
- The force that pushes electrons through a wire
- The material's opposition to the flow of charge

Quantity	Symbol	Unit of Measurement
Voltage	V	Volts (V)
Current	I	Amperes (A)
Resistance	R	Ohms (Ω)

2. Based on the table above, which unit is used to measure the 'push' or potential difference in a circuit?

$$V = I \times R$$

3. A circuit has a resistance of 10Ω and a current of 2 A. Calculate the voltage.

Electricity and Electrical Circuits: Current, Voltage, and Resistance

4. If a 12V battery is connected to a lightbulb and a current of 3A flows through it, what is the resistance of the bulb?

5. In a series circuit with three lightbulbs, what happens if one bulb burns out?

- The other two bulbs get brighter
- The other two bulbs stay lit
- All bulbs go out
- The battery explodes

6. What is a primary advantage of a parallel circuit in a home?

- It uses less wire than a series circuit
- Devices can be turned off independently without affecting others
- The total resistance increases as you add more devices
- It requires only one path for electricity

7. In a series circuit with a 9V battery and three identical bulbs, what is the voltage drop across each individual bulb?

Electricity and Electrical Circuits: Current, Voltage, and Resistance

8. Compare and contrast series and parallel circuits. Explain how the current behaves in each and why houses are wired in parallel.

9. In a circuit diagram, what does a straight line usually represent?

- A battery
- A switch
- A resistor
- An ideal connecting wire

10. Explain the difference between a conductor and an insulator, and provide one example of each.

Electricity and Electrical Circuits: Current, Voltage, and Resistance